

EE23BTECH11212 - MANUGUNTA MEGHANA SAI*

Question: A circuit containing a $80mH$ inductor and a $60\mu F$ capacitor in series is connected to a $230V$, $50Hz$ supply. A resistance of 15Ω is connected in series. Obtain the average power transferred to each element of the circuit, and the total power absorbed.

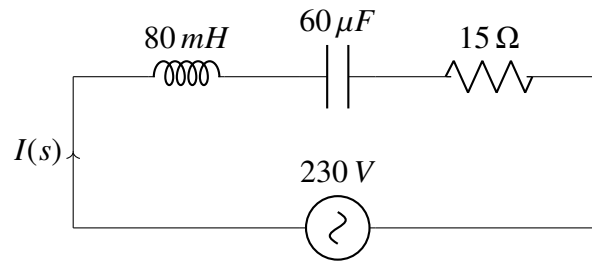


Fig. 1. LCR Circuit

Solution: In Fig. 1 the following information is provided:

Symbol	Value	Description
L	$80mH$	Inductance
C	$60\mu F$	Capacitance
R	15Ω	Resistance
V_{rms}	$230V$	Voltage
f	$50Hz$	Frequency
ω	$2\pi f = 100\pi$	Angular Frequency
ϕ	–	Phase difference between current and voltage
I_{rms}	–	rms value of current
V_m	–	Maximum voltage
I_m	–	Maximum current
P_m	–	Maximum Power

TABLE I
GIVEN PARAMETERS

Applying Kirchoff's Voltage Law in the Fig. 2

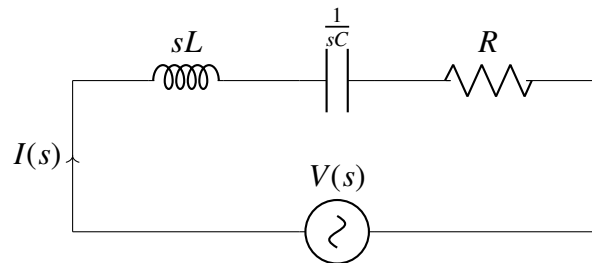


Fig. 2. s domain circuit

$$V(s) = RI(s) + sLI(s) + \frac{1}{sC}I(s) \quad (1)$$

$$= I(s) \left(R + sL + \frac{1}{sC} \right) \quad (2)$$

$$I(s) = \frac{V(s)}{\left(R + sL + \frac{1}{sC}\right)} \quad (3)$$

$$H(s) = \frac{V(s)}{I(s)} \quad (4)$$

$$H(s) = R + sL + \frac{1}{sC} \quad (5)$$

Substituting s with $j\omega$

$$H(j\omega) = R + j\omega L + \frac{1}{j\omega C} \quad (6)$$

$$\Rightarrow |H(j\omega)| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad (7)$$

Let the input voltage be:

$$V = V_m \sin(\omega t) \quad (8)$$

Let the current at a given instant be:

$$I = I_m \sin(\omega t - \phi) \quad (9)$$

Instantaneous power is given by:

$$P = VI \quad (10)$$

$$P = V_m \sin(\omega t) \times I_m \sin(\omega t - \phi) \quad (11)$$

Average power is given by:

$$P_{av} = \frac{W}{T} \quad (12)$$

$$dW = P dt \quad (13)$$

Integrating on both sides

$$W = V_m I_m \int_0^T \sin(\omega t) \sin(\omega t - \phi) dt \quad (14)$$

$$= V_m I_m \int_0^T \sin(\omega t) (\sin(\omega t) \cos(\phi) - \cos(\omega t) \sin(\phi)) dt \quad (15)$$

$$= V_m I_m \int_0^T (\sin(\omega t))^2 \cos(\phi) dt - V_m I_m \int_0^T \sin(\omega t) \cos(\omega t) \sin(\phi) dt \quad (16)$$

$$= V_m I_m \int_0^T \frac{1 - \cos(2\omega t)}{2} \cos(\phi) dt - V_m I_m \int_0^T \sin(2\omega t) \sin(\phi) dt \quad (17)$$

After solving the integral we get,

$$W = \frac{1}{2} V_m I_m T \cos \phi \quad (18)$$

Relation between V_{rms} and V_m :

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad (19)$$

Relation between I_{rms} and I_m :

$$I_{rms} = \frac{I_m}{\sqrt{2}} \quad (20)$$

a) The average power dissipated in a RLC circuit is given by :

$$P = V_{rms} I_{rms} \cos(\phi) \quad (21)$$

The phase difference is given by:

$$\tan(\phi) = \frac{\frac{1}{\omega C} - \omega L}{R} \quad (22)$$

After substituting the values from Table I:

$$\tan(\phi) = 1.86 \quad (23)$$

Rms value of current I_{rms} is given by :

$$I_{rms} = \frac{V_{rms}}{R} = \frac{230}{15} = 15.33A \quad (24)$$

Now, substituting the value of ϕ , I_{rms} and values from Table I in (21) we obtain the total power :

$$P_{av} = 789.62W \quad (25)$$

b) Average power transferred to the capacitor, P_C :

For a capacitor the phase angle is:

$$\phi = \frac{\pi}{2} \quad (26)$$

$$\cos(\phi) = 0 \quad (27)$$

$$P_C = 0 \quad (28)$$

c) Average power transferred to the inductor, P_L :

For an inductor the phase angle is:

$$\phi = -\frac{\pi}{2} \quad (29)$$

$$\cos(\phi) = 0 \quad (30)$$

$$P_L = 0 \quad (31)$$

d) Average Power transferred to the resistor, P_R :

$$P_{avg} = P_R + P_C + P_L \quad (32)$$

$$P_R = P_{avg} - P_C - P_L \quad (33)$$

$$P_R = 789.62 - 0 - 0 \quad (34)$$

$$P_R = 789.62W \quad (35)$$

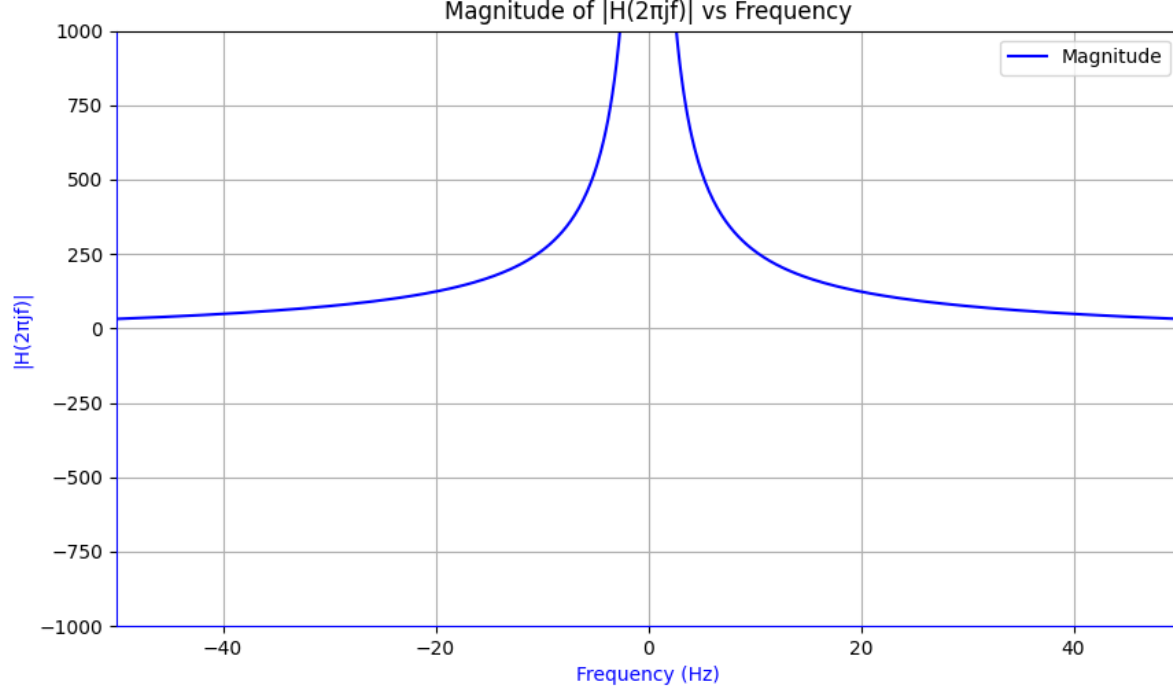


Fig. 3. $|H(j/\omega)|$ vs ω

Bandwidth is defined as the range of frequencies, where power ranges from its maximum value to half of its maximum value.

$$I_{rms} = \frac{V_{rms}}{|H(j\omega)|} \quad (36)$$

At maximum power, $|H(j\omega)|$ will be minimum,

$$|H(j\omega)| = R \quad (37)$$

$$I_m = \frac{V_{rms}}{R} \quad (38)$$

when, power is half of the maximum value of power

$$P = \frac{P_m}{2} \quad (39)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \quad (40)$$

$$|H(j\omega)| = \sqrt{2}R \quad (41)$$

$$\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{2}R \quad (42)$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2 \quad (43)$$

This equation has 2 roots, ω_1 and ω_2 :

$$\omega_1 = -\frac{R}{2L} + \sqrt{\frac{R^2}{4L} + \frac{1}{LC}} \quad (44)$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\frac{R^2}{4L} + \frac{1}{LC}} \quad (45)$$

Thus Bandwidth of circuit is :

$$\omega_2 - \omega_1 = \frac{R}{L} = 187.5 \quad (46)$$

$$f = \frac{\omega_2 - \omega_1}{2\pi} = 29.85 \quad (47)$$